



CS61C

Great Ideas
in
Computer Architecture
(a.k.a. Machine Structures)



Assistant
Teaching Professor
Lisa Yan

SDS IV/V: FSM, Blocks, ALU



Accumulator Circuit

- Accumulator Circuit
 - FSM
 - MUX: Data Multiplexor
 - Arithmetic Logic Unit (ALU)
-
- 1-Bit Adder
 - N-Bit Adder with Overflow
 - N-Bit Adder and Subtractor


Accumulator Example

- One more motivation for registers:




```
S_i = 0; // S_0
for (int i = 0; i < n; i++) {
    S_i = S_i + X_i;
}
```



 - Does this work?
- ✗ No!!! ✗**
 - We add X_i multiple times each clock cycle. Out of control!!



   Use a Register to "Pause." One Output per Cycle




- In the i -th iteration:
 - S_i is the input to the register and the result of the i^{th} iteration.
 - S_{i-1} is the register output and the result of the $(i-1)^{\text{th}}$ iteration.

i	0	1	2
S_{i-1}	0	<u>6</u>	<u>8</u>
X_i	6	2	3
S_i	<u>6</u>	<u>8</u>	11



Accumulator Waveform Diagram

 
The below waveform diagram shows we can speed up clock frequency!



Critical Path Determines Maximum Clock Frequency

- The minimum clock period is the delay on the **critical path**.
 - **Critical path:** The path between input(s) and output(s) that incurs worst-case (maximum) delay.
- Run the clock any faster, and your circuit becomes unstable!

 Max Delay of this Circuit =
Delay of Critical Path =
CLK-to-Q Delay
+ **CL Delay**
+ **Setup Time**





Summary: Timing Constraints

- A circuit that runs too fast can cause unstable outputs.
1. Set clock period to be (at minimum) the delay through the critical path.
 - **Critical path:** path between input/output that incurs max delay
 - Set maximum clock frequency = $1/(\text{minimum clock period})$
 2. [at home] Read about **hold time violations**
 - **Hold time violation:** fastest path between input/output is faster than register hold time (at input wire)





Practice

What is the maximum clock frequency for this circuit?

- A. 5 GHz
- B. 200 MHz
- C. 500 MHz
- D. 1/7 GHz
- E. 1/6 GHz
- F. Something else


clk-to-q delay: 1ns

setup time: 1ns

hold time: 1ns

AND delay: 1ns

 (Assume all unconnected inputs
come from some register.)





(pause)



How to build functions in hardware?




Finite State Machines

- Accumulator Circuit
 - FSM
 - MUX: Data Multiplexor
 - Arithmetic Logic Unit (ALU)
-
- 1-Bit Adder
 - N-Bit Adder with Overflow
 - N-Bit Adder and Subtractor

How to build functions in hardware?


- **Finite State Machine (FSM)**
 - A function that can be represented with a **"state transition diagram."**
 - Terminology on diagram
- (You may have seen FSMs in other classes)

 With combinational logic and registers, any FSM can be implemented in hardware.




3 Ones: Waveform Diagram

 - Function: Detect the occurrence of 3 consecutive 1's in the input.



-

 
How does the FSM (right) produce the waveform diagram (above)?



Hardware Implementation of FSM (1/2)




- Assume state transitions are controlled by the clock.
 - On each clock cycle the machine checks the inputs, then
 - It moves to a new state and produces a new output
- Each row of the **truth table** is one edge/transition.

PS	input	NS	output
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	00	0
10	1	00	1

 

Hardware Implementation of FSM (2/2)

   - A **register** is needed to remember which state the machine is in.
 - Use a **unique bit pattern** for each state.
- **Combinational logic circuit** implements a function that maps:
 - the input and present state (PS)
 - to the next state (NS) and output.






Agenda

MUX: Data Multiplexor

- Accumulator Circuit
 - FSM
 - MUX: Data Multiplexor
 - Arithmetic Logic Unit (ALU)
-
- 1-Bit Adder
 - N-Bit Adder with Overflow
 - N-Bit Adder and Subtractor

A New Block: Multiplexor

 - A **multiplexor (MUX)** is a basic logic function whose output is one of the inputs signals selected by a control signal.
 - Also called MUX; **Selector**
 - Implemented with logic gates.
- Example 1: 1-bit wide, 2-to-1 MUX



s	a	b	y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1


At home: Use sum-of-products to show MUX boolean expression

$$y = \bar{s}a + sb$$



MUX Terminology

 - Example 2: n -bit wide, 2-to-1 MUX
 - Data input A , B , output Y all n -bit wide
 - Control s : still 1-bit wide




- Example 3: A 32-bit wide 4-to-1 MUX
 - Selects between __ (1) __ input signals, each of which is __ (2) __ bits wide
 - Has __ (3) __ selector bits

- A.** 2
- B.** 4
- C.** 8
- D.** 16
- E.** 32
- F.** 64
- G.** 128
- H.** Something else




MUX Terminology

 - Example 2: n -bit wide, 2-to-1 MUX
 - Data input A , B , output Y all n -bit wide
 - Control s : still 1-bit wide



 - Example 3: A 32-bit wide 4-to-1 MUX
 - Selects between 4 input signals, each of which is 32 bits wide
 - Has 2 selector bits



S	s_1	s_0	Y
0	0	0	A
1	0	1	B
2	1	0	C
3	1	1	D




Arithmetic Logic Unit (ALU)

- Accumulator Circuit
 - FSM
 - MUX: Data Multiplexor
 - Arithmetic Logic Unit (ALU)
-
- 1-Bit Adder
 - N-Bit Adder with Overflow
 - N-Bit Adder and Subtractor

How do we build a Single-Core Processor?

 
Most Processors contain a special logic block called the **ALU (Arithmetic Logic Unit)**. The ALU performs arithmetic and bitwise operations.



Today, we will build a **simple 32-bit ALU** that supports 4 operations: AND, OR, ADD, SUBTRACT.

A Simple ALU


 
- Consider a Simple ALU:
 - Three inputs: 32-bit **A**, 32-bit **B**, and 2-bit input **S**
 - S selects the operation** to perform on A and B.
 - Outputs 32-bit **R**, the result of performing the selected operation on A and B.
- Suppose we consider 4 operations:
 - ADD
 - SUBTRACT
 - AND
 - OR



S		R
s_1	s_0	
0	0	A+B
0	1	A-B
1	0	A&B
1	1	A B

A Simple ALU

  In this circuit, **all results are computed** but exactly one is selected.



S		R
s_1	s_0	
0	0	A+B
0	1	A-B
1	0	A&B
1	1	A B



1-Bit Adder

- Accumulator Circuit
 - FSM
 - MUX: Data Multiplexor
 - Arithmetic Logic Unit (ALU)
-
- 1-Bit Adder
 - N-Bit Adder with Overflow
 - N-Bit Adder and Subtractor




Adder/Subtractor Design

Perform arithmetic with one block:

- **SUB** input bit: 1 if subtraction, 0 if addition
- **Overflow**: 1 if signed arithmetic overflow occurred

For now, we focus on **addition**.

 - Explore a design for an **n-bit adder**, where $n = 32, 4$, etc.





N-Bit Adder = Cascading Intuition

- For now, let's focus on **addition**.

- Consider adding two 4-bit numbers:

- $A = a_3 a_2 a_1 a_0$

- $B = b_3 b_2 b_1 b_0$

$$\begin{array}{cccc} c_3 & c_2 & c_1 & \\ a_3 & a_2 & a_1 & a_0 \\ + & b_3 & b_2 & b_1 & b_0 \\ \hline y_3 & y_2 & y_1 & y_0 \end{array}$$


- Addition in the i -th spot produces **two outputs**:
 - result** (e.g., y_i)
 - carry bit** (e.g., c_{i+1}) which feeds into the $(i+1)$ -th spot addition.

0110 carry bits

$$\begin{array}{r} 1011 \\ + 0001 \\ \hline 1100 \end{array}$$

N-Bit Adder = Cascading 1-Bit Adders
 
$$\begin{array}{r}
 c_3 \quad c_2 \quad c_1 \\
 a_3 \quad a_2 \quad a_1 \quad a_0 \\
 + \quad b_3 \quad b_2 \quad b_1 \quad b_0 \\
 \hline
 y_3 \quad y_2 \quad y_1 \quad y_0
 \end{array}$$




Instead of computing canonical form (e.g. via Sum Product), deconstruct our n-bit adder into a **cascade** of 1-bit adders.

"carry in" for
0-th spot

(1/4) One-bit Adder: 0-th Spot (without Carry In Bit)

a_0	b_0	y_0	c_1
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

	c_3	c_2	c_1	
	a_3	a_2	a_1	a_0
+	b_3	b_2	b_1	b_0
	y_3	y_2	y_1	y_0

 

$$y_0 = \text{XOR}(a_0, b_0)$$

$$c_1 = \text{AND}(a_0, b_0)$$

$$= a_0 b_0$$

XOR: 1 only if the #s of 1s at its input is odd.



	1	1		carry bits
	1	0	1	1
+	0	0	0	1
	1	1	0	0

(2/4) One-bit Adder: 1-th Spot (with Carry In Bit)

a_1	b_1	c_1	y_1	c_2
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$y_1 =$ _____

$c_2 =$ _____

  

- A.** $\text{XOR}(a_1, b_1)$
- B.** $\text{AND}(a_1, b_1)$
- C.** $\text{XOR}(a_1, b_1, c_1)$
- D.** $\text{AND}(a_1, b_1, c_1)$
- E.** $\text{MAJ}(a_1, b_1, c_1)$
(Majority bit)

F. Something else

(3/4) One-bit Adder: 1-th Spot (with Carry In Bit)

a_1	b_1	c_1	y_1	c_2
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1



$$y_1 = \text{XOR}(a_1, b_1, c_1)$$

$$c_2 = \text{MAJ}(a_1, b_1, c_1)$$

$$= a_1 b_1 + b_1 c_1 + a_1 c_1$$

XOR: 1 only if the #s of 1s at its input is odd.

MAJ ("majority"): see earlier

  

See notes for gate diagram



Agenda



N-Bit Adder with Overflow

- Accumulator Circuit
 - FSM
 - MUX: Data Multiplexor
 - Arithmetic Logic Unit (ALU)
-
- 1-Bit Adder
 - N-Bit Adder with Overflow
 - N-Bit Adder and Subtractor

Adder: Determining Overflow


Perform arithmetic with one block:

  - SUB input bit: 1 if subtraction, 0 if addition
- **Overflow**: 1 if signed arithmetic overflow occurred



How to compute overflow bit assuming that A, B are signed integers?

2-bit Signed Addition: Overflow (1/4)

 

A

11 "-1"				"-2"
10 "-2"			"0"	"1"
01 "1"		"-2"	"-1"	"0"
00 "0"	"0"	"1"	"-2"	"-1"
	00 "0"	01 "1"	10 "-2"	11 "-1"
+				

B

Boxed inputs incur signed overflow.

- c_{n-1} : carry in (e.g., c_1)
- c_n : carry out (e.g., c_2)

What is their relationship when overflow occurs? Doesn't occur?

- A.** $\text{AND}(c_n, c_{n-1})$
- B.** $\text{OR}(c_n, c_{n-1})$
- C.** $\text{NAND}(c_n, c_{n-1})$
- D.** $\text{NOR}(c_n, c_{n-1})$
- E.** $\text{XOR}(c_n, c_{n-1})$
- F.** Something else



11 "-1"				1 11 <u>+11</u> "-2" 110
10 "-2"			0 10 <u>+10</u> "0" 100	0 10 <u>+11</u> "1" 101
01 "1"		1 01 <u>+01</u> "-2" 010	0 01 <u>+10</u> "-1" 011	1 01 <u>+11</u> "0" 100
00 "0"	0 00 <u>+00</u> "0" 000	0 00 <u>+01</u> "1" 001	0 00 <u>+10</u> "-2" 010	0 00 <u>+11</u> "-1" 011
+	00 "0"	01 "1"	10 "-2"	11 "-1"

2-bit Signed Addition: Overflow (4/4)

Define "last stage" carry bits:

- c_{n-1} : carry in (e.g., c_1)
- c_n : carry out (e.g., c_2)

Relationship:

- Without overflow: $c_{n-1} = c_n$
- With overflow: $c_{n-1} \neq c_n$

overflow = XOR(c_n , c_{n-1})



Convince yourself this works for adding any n-bit signed integers!

11 "-1"				$\begin{array}{r} 1 \\ 11 \\ +11 \\ \hline "-2" \quad 110 \end{array}$
10 "-2"		$\begin{array}{r} 0 \\ 10 \\ +10 \\ \hline "0" \quad 100 \end{array}$	$\begin{array}{r} 0 \\ 10 \\ +11 \\ \hline "1" \quad 101 \end{array}$	
01 "1"	$\begin{array}{r} 1 \\ 01 \\ +01 \\ \hline "-2" \quad 010 \end{array}$	$\begin{array}{r} 0 \\ 01 \\ +10 \\ \hline "-1" \quad 011 \end{array}$	$\begin{array}{r} 1 \\ 01 \\ +11 \\ \hline "0" \quad 100 \end{array}$	
00 "0"	$\begin{array}{r} 0 \\ 00 \\ +00 \\ \hline "0" \quad 000 \end{array}$	$\begin{array}{r} 0 \\ 00 \\ +01 \\ \hline "1" \quad 001 \end{array}$	$\begin{array}{r} 0 \\ 00 \\ +10 \\ \hline "-2" \quad 010 \end{array}$	$\begin{array}{r} 0 \\ 00 \\ +11 \\ \hline "-1" \quad 011 \end{array}$
+	00 "0"	01 "1"	10 "-2"	11 "-1"

Adder: Overflow is XOR of Carry Bits

Perform arithmetic with one block:

  - SUB input bit: 1 if subtraction, 0 if addition
- **Overflow**: 1 if signed arithmetic overflow occurred






N-Bit Adder and Subtractor

- Accumulator Circuit
 - FSM
 - MUX: Data Multiplexor
 - Arithmetic Logic Unit (ALU)
-
- 1-Bit Adder
 - N-Bit Adder with Overflow
 - N-Bit Adder and Subtractor

Adder/Subtractor Design

Perform arithmetic with one block:

 - **SUB** input bit: 1 if subtraction, 0 if addition
- **Overflow**: 1 if signed arithmetic overflow occurred



Signed integers
with two's
complement!

SUB signals add or subtract:



$$0: Y = A + B$$

$$1: Y = A + (-B)$$

$$= A + \underbrace{\sim B + 1}_{\text{bitwise inversion}}$$

bitwise
inversion

  Subtractor Design: Extremely Clever! (1/2)



SUB signals add or subtract:

$$0: Y = A + B$$

$$1: Y = A + (-B)$$

$$= A + (\sim B + 1)$$



$$c_0 = \text{SUB}$$

Yan, SP26

Subtractor Design: Extremely Clever! (2/2)

XOR is a conditional inverter! [See notes](#)

SUB	XOR(SUB, 0)	XOR(SUB, 1)	
0	0	1	pass through
1	1	0	invert

 
 


SUB signals add or subtract:

$$\begin{aligned}
 0: Y &= A + \mathbf{B} \\
 1: Y &= A + (-B) \\
 &= A + (\underbrace{\sim \mathbf{B} + 1}_{\text{XOR with SUB}})
 \end{aligned}$$

XOR with SUB

N-Bit Adder/Subtractor, Summary

  

SUB signals add or subtract:

$$0: Y = A + B$$

$$1: Y = A + (-B)$$

$$= A + (\sim B + 1)$$

"And In conclusion..."

- Use muxes to select among input
 - S input bits selects 2^S inputs
 - Each input can be n -bits wide, indep of S
- Can implement muxes hierarchically
- ALU can be implemented using a mux
 - Coupled with basic block elements
- N -bit adder-subtractor done using N 1-bit adders with XOR gates on input
 - XOR serves as conditional inverter

