



CS61C

Great Ideas
in
Computer Architecture
(a.k.a. Machine Structures)



Assistant Teaching
Professor
Lisa Yan

RISC-V Datapath I

Great Idea #1: Abstraction (Levels of Representation/Interpretation)



High Level Language
Program (e.g., C)

```
temp = v[k];
v[k] = v[k+1];
v[k+1] = temp;
```

Compiler

Assembly Language
Program (e.g., RISC-V)

```
lw    x3, 0(x10)
lw    x4, 4(x10)
sw    x4, 0(x10)
sw    x3, 4(x10)
```

Assembler


Machine Language
Program (RISC-V)

```
1000 1101 1110 0010 0000 0000 0000 0000
1000 1110 0001 0000 0000 0000 0000 0100
1010 1110 0001 0010 0000 0000 0000 0000
1010 1101 1110 0010 0000 0000 0000 0100
```

Hardware Architecture Description
(e.g., block diagrams)

Architecture Implementation

 
Logic Circuit Description
(Circuit Schematic Diagrams)



How do we build a Single-Core Processor?

Processor (CPU): the active part of the computer that does all the work (data manipulation and decision-making).

 - **Datapath** (“the brawn”): portion of the processor that contains hardware necessary to perform operations required by the processor.
- **Control** (“the brain”): portion of the processor (also in hardware) that tells the datapath what needs to be done.



5 Steps to a RISC-V Instruction


- 5 Steps to a RISC-V Instruction
- R-Type: **add** datapath
- R-Type: **sub** datapath
- I-Type: **addi** datapath
- Supporting Loads and Stores
- Designing the Immediate Generation Block
- [Reference] CPU Elements

What Key CPU Elements Do We Need?

In each clock cycle, RV32I instruction data passes through these elements.

- ALU, Read State: Combinational logic with delay
- Write state: **rising-edge triggered** with clock

Read the notes for details!

 

5 Basic Steps (“Stages”) of Instruction Execution


1. Instruction
Fetch (**IF**)

2. Instruction
Decode (**ID**)
+ Read Registers

3. Execute (**EX**)
Arithmetic Logic
Unit (ALU)

4. Memory
Access (**MEM**)


5. Write back
to Register (**WB**)

 

- **Modularity: Break up the process into steps**
 - Easy to optimize one stage without touching the others

Mission Control (Control Logic)

 - MUX selector, ALU op selector, write enable, etc.
- Control Logic specifies which instruction to execute.



Control and Datapath are two *abstractions* that together comprise the CPU. Under the hood, both are designed with combinational logic and/or state elements.

Our Plan: Iteratively Build Processor

In each clock cycle, RV32I instruction data passes through these elements.

- ALU, Read State: Combinational logic with delay
- Write state: **rising-edge triggered** with clock

Read the notes for details!

Which elements are “clocked,” i.e., synchronous state elements?



Control Logic




Yan, SP26




Your Own Design

1. We should use the main ALU to compute $PC=PC+4$ in order to save some gates.
2. The ALU is a **synchronous state element**.
3. The program counter (PC) is a **register**.


FFF

 


FFT

 

FTF

 


FTT

 

TFF




TFT

 

TTF



TTT

 

Your Own Design

1. We should use the main ALU to compute $PC = PC + 4$ in order to save some gates.
2. The ALU is a synchronous state element.
3. The program counter (PC) is a register.

	1	2	3
A.	F	F	F
B.	F	F	T
C.	F	T	F
D.	F	T	T
E.	T	F	F
F.	T	F	T
G.	T	T	F
H.	T	T	T

*synchronous state element are clocked.

Not all state elements are clocked; some like IMEM operate like combinational logic!



R-Type: **add** Datapath

- 5 Steps to a RISC-V Instruction
- R-Type: **add** datapath
- R-Type: **sub** datapath
- I-Type: **addi** datapath
- Supporting Loads and Stores
- Designing the Immediate Generation Block
- [Reference] CPU Elements



Implementing the add Instruction

- Suppose we had a single instruction in our RISC-V ISA: add.

add rd rs1 rs2

Example add-only program

0x100		add x18 x18 x10
0x104		add x18 x18 x18
...		add ...

- The add instruction makes **two changes** to processor state:

- RegFile
- PC

$$R[rd] = R[rs1] + R[rs2]$$
$$PC = PC + 4$$

Our Plan: Iteratively Build Processor

For now, we will disconnect memory.
By the end of next lecture, we'll build the datapath that supports the full RV32I ISA.



Control Logic

Datapath for add

$$PC = PC + 4$$


$$R[rd] = R[rs1] + R[rs2]$$

Increment PC to next instruction.

Split instruction to index into RegFile.

Feed read register values into Add.

 Write Add output to destination register.



Control Logic

RegWEn
1



R-Type: `sub` Datapath

- 5 Steps to a RISC-V Instruction
- R-Type: `add` datapath
- R-Type: `sub` datapath
- I-Type: `addi` datapath
- Supporting Loads and Stores
- Designing the Immediate Generation Block
- [Reference] CPU Elements

Implementing the sub Instruction

- What if our ISA now had two instructions: add/sub?

sub rd rs1 rs2

- sub is almost the same as add, except now the ALU **subtracts**:

- RegFile $R[rd] = R[rs1] - R[rs2]$

- PC $PC = PC + 4$

- Control logic* changes!



Datapath for sub

31	25	24	20	19	15	14	12	11	7	6	0					
0 <u>1</u> 00000				rs2			rs1			funct3		rd		0110011		

$$PC = PC + 4$$


$$R[rd] = R[rs1] - R[rs2]$$

Increment PC to next instruction.

Split instruction to index into RegFile.

Feed read register values into ALU.

 Write *ALU output* to destination register.



funct7			funct3		opcode	
0000000	rs2	rs1	000	rd	0110011	add
0100000	rs2	rs1	000	rd	0110011	sub
0000000	rs2	rs1	001	rd	0110011	sll
0000000	rs2	rs1	010	rd	0110011	slt
0000000	rs2	rs1	011	rd	0110011	sltu
0000000	rs2	rs1	100	rd	0110011	xor
0000000	rs2	rs1	101	rd	0110011	srl
0100000	rs2	rs1	101	rd	0110011	sra
0000000	rs2	rs1	110	rd	0110011	or
0000000	rs2	rs1	111	rd	0110011	and



ALUSel
add,sub,xor,and,or,sl
t,sltu,sll,sra,srl

The **Control Logic** decodes **funct3**, **funct7** instruction fields and selects appropriate **ALU** function by setting the control line **ALUSel**.



I-Type: `addi` Datapath

- 5 Steps to a RISC-V Instruction
- R-Type: `add` datapath
- R-Type: `sub` datapath
- I-Type: `addi` datapath
- Supporting Loads and Stores
- Designing the Immediate Generation Block
- [Reference] CPU Elements

Implementing the addi Instruction

- Suppose we add a new instruction: `addi`, RV32I I-Type:

`addi rd rs1 imm`

- The `addi` instruction updates the same two states as before.

But we now need to build an immediate `imm`!

- RegFile


$$R[rd] = R[rs1] + imm$$

- PC

$$PC = PC + 4$$

1. New MUX to Select Immediate for ALU

 
1. Control line BSel=1 selects the generated immediate `imm` for ALU input B.



2. New Block to Generate 32-bit Immediate

2. Immediate Generation Block builds a 32-bit immediate **imm** from instruction bits.

 1. Control line BSel=1 selects the generated immediate **imm** for ALU input B.




Tracing/Lighting the addi Datapath

Increment PC to next instruction.

Immediate Generation Block builds a 32-bit immediate **imm** from instruction bits.

Control line **Bsel=1** selects the generated immediate **imm** for ALU input B.

 Write ALU output to destination register.



Data `inst[24:20]` still feeds into RegFile, which still outputs `R[rs2]`.
However, control `Bsel=1` means `R[rs2]` data line is *ignored*.



Yan, SP26

Supporting Loads & Stores

- 5 Steps to a RISC-V Instruction
- R-Type: **add** datapath
- R-Type: **sub** datapath
- I-Type: **addi** datapath
- Supporting Loads and Stores
- Designing the Immediate Generation Block
- [Reference] CPU Elements




Implementing the `lw` Instruction

- `lw` uses **I-Type**: `lw rd imm(rs1)`
- Similar datapath to `addi`, but creates an address (not the final value stored).
$$\text{addr} = (\text{Base register } rs1) + (\text{sign-extended } imm \text{ offset})$$
- State element access now includes a **memory read**!
 - DMem (read word at address `addr`)
 - RegFile `R[rs1] # read; R[rd] # write`
 - PC `PC = PC + 4`

Saving Memory Read to RegFile

Read memory at address
 $alu = R[rs1] + imm.$

 If load instruction, save **mem**.
 Otherwise, save **alu**.





Lighting the LOAD Datapath

Load uses all five stages of the datapath!


Increment PC to next instruction.

*Immediate Generation Block builds a 32-bit immediate **imm**.*

ALU computes address **alu** = $R[rs1] + imm$.

Read memory at address **alu**.

 Write loaded memory value **mem** to register.





Designing the Immediate Generation Block

- 5 Steps to a RISC-V Instruction
- R-Type: `add` datapath
- R-Type: `sub` datapath
- I-Type: `addi` datapath
- Supporting Loads and Stores
- Designing the Immediate Generation Block
- [Reference] CPU Elements



[Review] Swirl Immediate Bits around for HW Design

- Recall RISC-V keeps read/write register fields consistent across instruction formats.
- RISC-V also tries to keep **bit positions of immediates** consistent:


	31	26	24	20	19	15	14	12	11	7	6	0
I-Type	imm[11:0]					rs1	funct3	rd			opcode	
	imm[11:5]			imm[4:0]								
	yXXXXXXXX			WWWWV		10011						
S-Type	imm[11:5]			rs2	rs1	funct3	imm[4:0]			opcode		
	VXXXXXXXX						WWWWV					
	imm[12 10:5]			rs2	rs1	funct3	imm[4:1 11]			opcode		
B-Type	zXXXXXXXX						WWWwy					






I-Type Immediate

GOT TO HERE

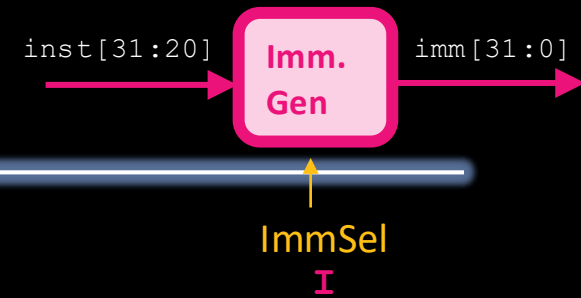

Instruction

inst[31:0]

 

Copy upper 12 bits of instruction, **inst[31:20]**, to lower 12 bits of immediate, **imm[11:0]**.

Immediate


imm[31:0]

Sign-extend: Copy **inst[31]** to upper 20 bits of immediate, **imm[31:12]**.






S-Type Immediate (1/2)

 

Instruction `inst[31:0]`

	31	30	25	24	20	19	15	14	12	11	7	6	0
I-Type	imm[11 10:5]					rs2		rs1	funct3	rd	I-OPCODE		
S-Type	imm[11 10:5]					rs2		rs1	funct3	imm[4:0]	S-OPCODE		

 

Immediate `imm[31:0]`



	31	30	25	24	20	19	15	14	12	11	7	6	S	0
I-Type	imm[11 10:5]				imm[4:0]		rs1		funct3		rd		I-OPCODE	
S-Type	imm[11 10:5]				rs2		rs1		funct3		imm[4:0]		S-OPCODE	





`instr[31]` is always the sign bit.

MUX for `imm[11]`:

- S: instr[31]
- B: instr[7]

MUX for `imm[0]`:

- S: `instr[7]`
- B: 0 (implicit 0; half-words → bytes)



Immediate imm[31:0]



Read the notes!!


[Reference] CPU Elements

- 5 Steps to a RISC-V Instruction
- R-Type: **add** datapath
- R-Type: **sub** datapath
- I-Type: **addi** datapath
- Supporting Loads and Stores
- Designing the Immediate Generation Block
- [Reference] CPU Elements


Combinational Logic Blocks, State Elements

Logic subcircuits as block diagrams:

Last time

 


1-bit-wide 2-to-1 MUX

 


Simple ALU (add,sub,and,or)

This time

 


32-bit-wide 2-to-1 MUX

 

ALU (ALUOp selects from multiple operations)
21-RISC V Datapath I (41)

State elements:


 


Within a clock cycle:

- Combinational logic updates occur after delay through the block.
- State element updates occur on the **next** rising clock edge.

State Elements (1/3): Program Counter

Program
Counter

  

A register in Logisim

The Program Counter
is a **32-bit Register**.

Register
File Reg



Memory
MEM



- Input:
 - N-bit data input bus
 - Write Enable** “Control” bit (1: asserted/high, 0: deasserted/0)
- Output:
 - N-bit data output bus
- Behavior:
 - If Write Enable is 1 on *rising clock edge*, set Data Out=Data In.
 - At all other times, Data Out will not change; it will output its current value.

State Elements (2/3): Register File


Program Counter



Register File Reg



Memory MEM

 

Register File (**RegFile**) has 32 registers.

■ Input:

- One 32-bit input data bus, *wdata*.
- Three 5-bit select busses, *rs1*, *rs2*, and *rd*.
- **RegWEn** control bit.

■ Output:

- Two 32-bit output data busses, *rdata1* and *rdata2*.

■ Registers are accessed via their 5-bit register numbers:

- **R[rs1]**: *rs1* selects register to put on *rdata1* bus out.
- **R[rs2]**: *rs2* selects register to put on *rdata2* bus out.
- **R[rd]**: *rd* selects register to be written via *wdata* when **RegWEn**=1.

■ Clock behavior: Write operation occurs on *rising clock edge*.

■ Clock input only a factor on write!

■ All read operations behave like a combinational block:

- If *rs1*, *rs2* valid, then *rdata1*, *rdata2* valid after *access time*.

For read operations (RegWEn=1), RegFile behaves like a combinational block.

State Elements (3/3): Memory


Program Counter



Register File Reg



Memory MEM

 

Memory is “magic.” For this class:

- 32-bit byte-addressed memory space; and
- Memory access with 32-bit words.

- Memory words are accessed as follows:
 - Read: Address *addr* selects word to put on *rdata* bus.
 - Write: Set **MemRW=1**. Address *addr* selects word to be written with *wdata* bus.
- Like RegFile, **clock input** is only a factor on write.
 - If MemRW=1, write occurs on rising clock edge.
 - If MemRW=0 and *addr* valid, then *rdata* valid after access time.

For read operations (MemRW=0), memory behaves like a combinational logic block.

“Two” Memories: IMEM, DMEM


Program
Counter



Register
File Reg



Memory
MEM

 

- Current abstraction: Memory holds both instructions and data in one contiguous 32-bit memory space.
- In our processor, we'll use two “separate” memories:
 - IMEM:** A *read-only* memory for fetching instructions.
 - DMEM:** A memory for loading (read) and storing (write) data words.
 - Under the hood, these are placeholders for L1 caches: **L1i**, **L1d**.
- IMEM is read-only and therefore always behaves like a combinational block.